

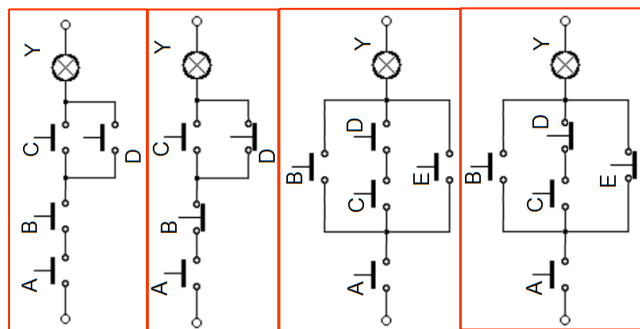
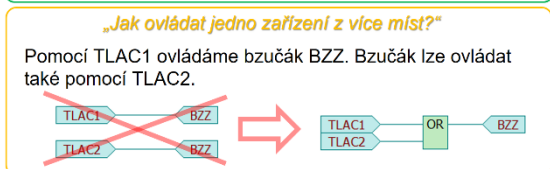


„Jiné“ použití funkcí AND / OR

A	B	AND a zároveň	OR nebo
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	1

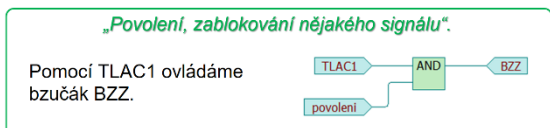

A	B	AND a zároveň	OR nebo	NOT B	NAND	NOR	XOR neshoda	XNOR shoda
0	0	0	0	1	1	1	0	1
0	1	0	1	0	1	0	1	0
1	0	0	1	1	1	0	1	0
1	1	1	1	0	0	0	0	1

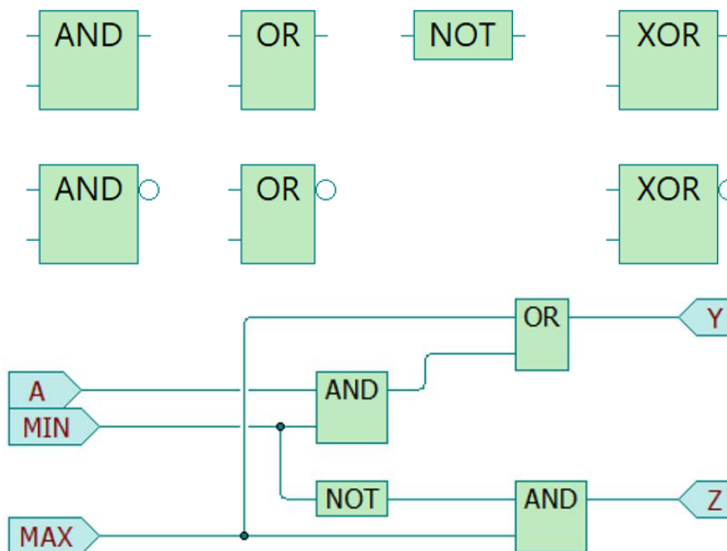

Jak skutečně připojit k PLC externí zařízení?

